

**Isolated 0-10V to 4-20mA
Converter Application**



Industrial controllers and data acquisition equipment frequently require an isolated voltage-to-current loop converter in environments where high common mode noise exist and protection of equipment and personnel from high voltages are required. The current loop, usually 4-20mA, is used to drive control valves or the input to chart recorders for temperature/pressure monitoring over time for example. Figure 1 shows a simplified block diagram of an isolated pressure transmitter.

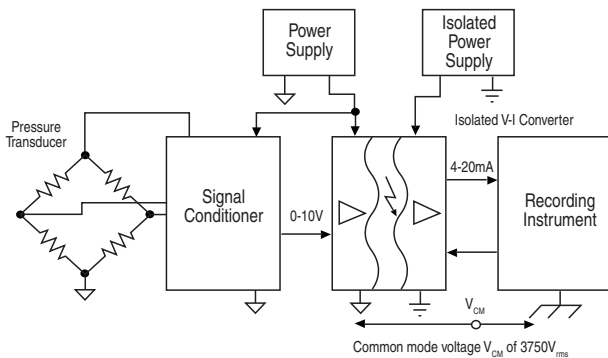


Figure 1. Isolated Pressure Transmitter

The LIA100P, with a typical Common Mode Rejection Ratio of 130dB (see Figure 1A) and isolation voltage up to 3750V is a good choice for this kind of application.

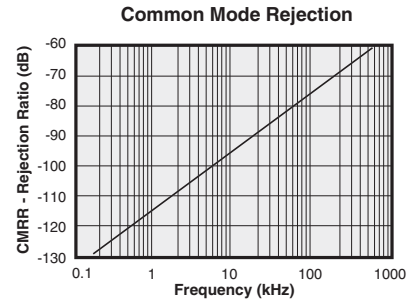


Figure 1A.

The example circuit for this application is shown in figure 1B.

The LIA110P is in the photovoltaic mode which has linearity comparable to a 13-14 bit D/A converter with 1 LSB nonlinearity or 0.01% of full scale. The result is a clean, linear conversion from 0-10V to 4-20mA as shown in figure 2.


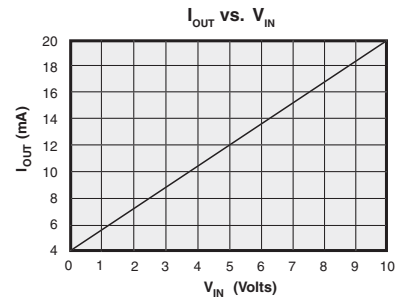


Figure 2.

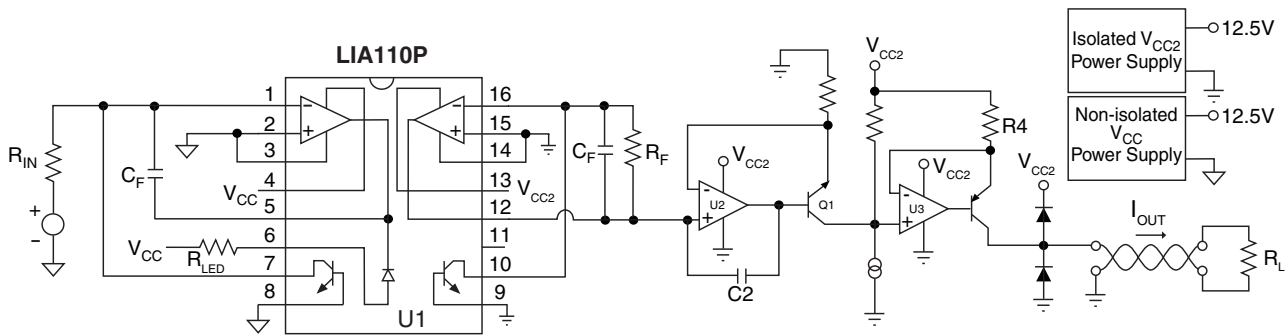

Note: For single power supply: $\nabla = V_{EE1}$ $\nabla = V_{EE2}$

Figure 1B. 0-10V to 4-20mA Converter

For additional information please visit our website at: www.ixysic.com

IXYS Integrated Circuits Division makes no representations or warranties with respect to the accuracy or completeness of the contents of this publication and reserves the right to make changes to specifications and product descriptions at any time without notice. Neither circuit patent licenses nor indemnity are expressed or implied. Except as set forth in IXYS Integrated Circuits Division's Standard Terms and Conditions of Sale, IXYS Integrated Circuits Division assumes no liability whatsoever, and disclaims any express or implied warranty, relating to its products including, but not limited to, the implied warranty of merchantability, fitness for a particular purpose, or infringement of any intellectual property right.

The products described in this document are not designed, intended, authorized or warranted for use as components in systems intended for surgical implant into the body, or in other applications intended to support or sustain life, or where malfunction of IXYS Integrated Circuits Division's product may result in direct physical harm, injury, or death to a person or severe property or environmental damage. IXYS Integrated Circuits Division reserves the right to discontinue or make changes to its products at any time without notice.